

Lecture 13, Oct 6, 2022

More on Flip-Flops

- D-flip flops can be positive edge or negative edge triggered
 - A negative edge triggered D-flip flop is basically a positive one but with clock inverted; it stores a value on a clock negative edge (1 to 0)
- A latch tracks changes in its input as long as the clock is high, but a flip-flop only tracks changes on a positive or negative clock edge (transition)
 - D needs to be stable for some time (set-up time) before the clock changes, otherwise the flip-flop ends up in a *metastable state*, so D and clock can't change at the same time
- In Verilog `register` is a flip flop

Verilog Code for Sequential Circuits

- For a D-latch:

```
module D_latch(input logic D, clk,
              output logic Q);
    always_latch
        if (clk == 1)
            Q = D;
endmodule
```

- The `always_latch` makes it a latch
- If a `case` or `if` does not cover all cases, the compiler will infer a latch, i.e. it stores the previous value
 - In this case that's exactly what we want – we have no `else`, so the compiler creates a latch to store the previous value of D and assign it to Q
- For a flip-flop:

```
module D_FF(input logic D, clk,
            output logic Q);
    always_ff @(posedge clk)
        Q <= D;
endmodule
```

- `posedge` is a keyword that means the flip flop should trigger on the positive edge
 - `negedge` is a negative edge trigger
- `always_ff` creates a flip flop
- When code describes flip flops, the assignments should use `<=`, not `=`
 - `<=` is a nonblocking assignment used for sequential logic
 - `=` is a blocking assignment used for combinational logic
- The stuff inside `always_ff` only executes on a positive edge, so we don't need an `if` (whereas the latch needs to check)
- For an 8-bit register (in the schematic it's denoted by a D-flip flop with an 8-bit bus for D and Q):

```
module reg8(input logic [7:0] D,
            input logic clk,
            output logic [7:0] Q);
    always_ff @(posedge clk)
        Q <= D;
endmodule
```

- Note the only difference is D and Q are now buses, but inside the module the code is identical since we assign all 8 bits at once

Resets

- How do we reset a flip-flop to a known value?
 - Synchronously (on a clock edge) or asynchronously (independent of clock edge)
- In the synchronous case we can AND together D and a reset signal and then feed into the flip flop
 - This is known as an *active-low* reset because when the reset signal is 0, the value is reset

 


Figure 1: Synchronous reset D-flip flop

 


Figure 2: Synchronous reset D-flip flop symbol

```
module D_FF(input logic D, clk, resetn,  
            output logic Q);  
    always_ff @(posedge clk)  
        if (resetn == 0)  
            Q <= 1'b0;  
        else  
            Q <= D;  
end
```

- In the asynchronous case, the flip-flop can be reset regardless of the clock
- Regardless of the state of the clock, as long as reset is 0, Q will be reset
- Asynchronous reset is marked by an AR instead of just R

 


Figure 3: Asynchronous reset D-flip flop